

Chapter 2: Boolean Algebra & Logic Gates

→

Ex - OR :-



A	B	$Y = A \oplus B \Rightarrow [A\bar{B} + \bar{A}B]$
0	0	0
0	1	1
1	0	1
1	1	0

↑
Ex-NOR

Ex - NOR :-



* Postulates & Theorems :- [Boolean]
↳ 0/1

- Postulate 2 (a) $x + 0 = x$ (b) $x \cdot 1 = x$
 " (a) $\frac{x + x'}{x + \bar{x}} = 1$ (b) $\frac{x \cdot x'}{x \cdot \bar{x}} = 0$
 Theorem 1 (a) $\frac{x + x}{[x \text{ OR } x]} = x$ (b) $x \cdot x = x$
 Theorem 2 (a) $x + 1 = 1$ (b) $x \cdot 0 = 0$
 Theorem 3 $\rightarrow (x')' = x$ [Circuit diagram showing a variable x passing through two inverters to return to x]

Postulate 3
(Commutative)

Theorem 4
Associative

Distributive

Theorem 5
De Morgan

Theorem 6
Absorption

- (a) $x + y = y + x$ (b) $xy = yx$
 (a) $x + (y + z) = (x + y) + z$ (b) $x(yz) = (xy)z$
 (a) $x(y + z) = xy + xz$ (b) $x + yz = \frac{(x + y)(x + z)}{1}$
 (a) $(x + y)' = x' \cdot y'$ (b) $(xy)' = x' + y'$
 (a) $x + xy = x$ (b) $x(x + y) = x$

Proof :-

$$\text{LHS} = x + yz \quad \& \quad \text{RHS} = (x + y)(x + z)$$

$$= x \cdot x + x \cdot z + x \cdot y + y \cdot z$$

$$= [x + x \cdot y + x \cdot z] + y \cdot z$$

$$= x[1 + y + z] + yz$$

① Logical Equations \Rightarrow

$$= x \cdot 1 + yz$$

$$= x + yz = \text{LHS}$$

② Truth Table method:

x	y	z	$f_1 = y \cdot z$	<u>LHS</u> ✓ $f_2 = x + yz$	$f_3 = x + y$	$f_4 = x + z$	<u>RHS</u> ✓ $f_5 = f_3 \cdot f_4$
0	0	0	0	0	0	0	0
0	0	1	0	0	0	1	0
0	1	0	0	0	1	0	0
0	1	1	1	1	1	1	1
1	0	0	0	1	1	1	1
1	0	1	0	1	1	1	1
1	1	0	0	1	1	1	1
1	1	1	1	1	1	1	1

Absorption

$$\text{LHS} = x + xy =$$

$$= x(1 + y)$$


$$= \underline{x = \text{RHS}}$$

* De - Morgan's Theorem :-

Statement 1: "The complement of a sum is equal to the product of complements of each variable individually."

$$\checkmark \left[\overline{(A+B)} \right]_{\text{NOR}} = \overline{A \cdot B}_{\text{Bubble AND}}$$
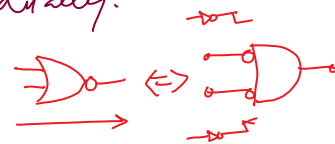
$$\checkmark \left[\overline{(A+B+C)} \right] = \overline{A \cdot B \cdot C}$$




$$\overline{(A+B+C+\dots+N)} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \dots \cdot \overline{N}$$

A	B	A+B	<u>LHS</u> $\overline{A+B}$	\overline{A}	\overline{B}	<u>RHS</u> $\overline{A \cdot B}$
0	0	0	1	1	1	1
0	1	1	0	1	0	0
1	0	1	0	0	1	0
1	1	1	0	0	0	0

Statement 2: "Complement of a product is equal to sum of complements of individual variables."

sum of complements of individual variables.
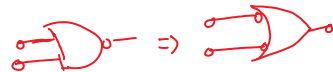
$$\underbrace{(A \cdot B)}_{\text{NAND}} = \underbrace{\overline{A + B}}_{\text{Bubbled OR}} \Rightarrow$$



$$\overline{(A \cdot B \cdot C)} = \overline{A} + \overline{B} + \overline{C}$$

$$\overline{(A \cdot B \cdot C \cdot \dots \cdot N)} = \overline{A} + \overline{B} + \overline{C} + \dots + \overline{N}$$

* Canonical & standard Forms :-

↳ Minterms & Maxterms

Dec.	A	B	(AND) minterms = (1)	(OR) Maxterm
0	0	0	$m_0 = \overline{A}\overline{B}$	$M_0 = A + B$
1	0	1	$m_1 = \overline{A}B$	$M_1 = A + \overline{B}$
2	1	0	$m_2 = A\overline{B}$	$M_2 = \overline{A} + B$
3	1	1	$m_3 = AB$	$M_3 = \overline{A} + \overline{B}$

A	B	C	minterms	Maxterms
0	0	0	$m_0 = \overline{A} \cdot \overline{B} \cdot \overline{C}$	$M_0 = A + B + C$
0	0	1	$m_1 = \overline{A} \cdot \overline{B} \cdot C$	$M_1 = A + B + \overline{C}$
.
.
.

$$1 \ 1 \ 1 \leftarrow m_7 = \overline{A} \cdot \overline{B} \cdot \overline{C} \quad M_7 = A + B + C$$

→ Canonical Forms :- $F_2 = (AB) + (\overline{A}B\overline{C}) \Rightarrow$ standard form
 $F_1(A, B, C) = \underline{A} + \underline{BC} \Rightarrow$ standard form

- ↳ (1) Sum of minterms =
 (2) Product of maxterms

Ex.1 Derive the canonical form in terms of sum of minterms.

$$\begin{aligned} F_1(A, B, C) &= A + BC \\ &= A \cdot \underline{1} + BC \cdot \underline{1} \\ &= A(B + \overline{B}) + BC(A + \overline{A}) \end{aligned}$$

$$AB \cdot (1) \uparrow \\ AB \cdot (C + \bar{C})$$

$$= AB + A\bar{B} + A\bar{B}C + \bar{A}B\bar{C} \\ = \underbrace{AB(C + \bar{C})}_{\substack{111 \\ 110}} + \underbrace{A\bar{B}(C + \bar{C})}_{\substack{101 \\ 100}} + \underbrace{\bar{A}B\bar{C}}_{\substack{011 \\ 010}} \\ = \underbrace{ABC + AB\bar{C}}_{\substack{111 \\ 110}} + \underbrace{A\bar{B}C + A\bar{B}\bar{C}}_{\substack{101 \\ 100}} + \underbrace{\bar{A}B\bar{C}}_{\substack{011 \\ 010}} \\ = m_7 + m_6 + m_5 + m_4 + \underbrace{m_3}_{\substack{011 \\ 010}} + m_2$$

$$= m_3 + m_4 + m_5 + m_6 + m_7 \\ A + BC \rightarrow F(A, B, C) = \sum (3, 4, 5, 6, 7)$$

$$(2) F_2(A, B, C) = \bar{A}\bar{B} + \bar{C} = \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} \\ + A\bar{B}\bar{C} + ABC \\ = \sum (0, 2, 4, 5, 6) \checkmark$$

$$(3) F(A, B, C, D) = \bar{A}\bar{B} + \bar{C}D = \sum (1, 5, 8, 9, 10, 11, 13)$$

[B] Product of Maxterms:-

Maxterms are complement of minterms

Find out the maxterms for the function:

$$F_1 = A + BC$$

minterm \rightarrow Maxterm

$$A + B + \underline{0}$$

Apply distributive law

$$= (A + B) \cdot (A + C)$$

$$= (A + B + 0) (A + C + 0)$$

$$= (\underbrace{A + B + C \cdot \bar{C}}_{\substack{111 \\ 110}}) (\underbrace{A + C + B \cdot \bar{B}}_{\substack{101 \\ 100}})$$

$$= \underbrace{(A + B + C)}_{\substack{000 \\ 001}} \underbrace{(A + B + \bar{C})}_{\substack{000 \\ 010}} \underbrace{(A + \bar{B} + C)}_{\substack{000 \\ 010}}$$

$$= M_0 \cdot M_1 \cdot M_2 \cdot M_2$$

$$= M_0 \cdot M_1 \cdot M_2$$

$$F_1 = A + BC = \prod (0, 1, 2) = \sum (3, 4, 5, 6, 7)$$

A	B	C	Maxterms / Minterms	BC	A + BC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
1	1	1	1	1	1

0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

0	0
0	0
1	1
0	1
0	1
0	1
1	1

Ex. 2

Find out the minterms for following function:-

$$F_1 = A\bar{B} + C\bar{D}$$

$$= (A\bar{B} + C)(A\bar{B} + \bar{D})$$

$$= (A+C)(\bar{B}+C)(A+\bar{D})(\bar{B}+\bar{D})$$

$$= (A+C+B\bar{B})(A\bar{A}+\bar{B}+C)(A+\bar{D}+B\bar{B})$$

$$= (A+B+C)(A+\bar{B}+C)(A+\bar{B}+C)(A+\bar{B}+\bar{D})$$

$$= (A+B+C+\bar{D}\bar{D})(A+\bar{B}+C+\bar{D}\bar{D})(A+\bar{B}+C+\bar{D}\bar{D})$$

$$(A+B+\bar{D}+\bar{C}\bar{C})(A+\bar{B}+\bar{D}+\bar{C}\bar{C})(A+\bar{B}+\bar{D}+\bar{C}\bar{C})$$

$$= (A+B+C+D)(A+B+C+\bar{D})(A+\bar{B}+C+D)$$

$$(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)(\bar{A}+\bar{B}+C+\bar{D})$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

$$(A+\bar{B}+C+D)(A+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+C+D)$$

Standard forms
↓
Canonical forms

* Standard forms:-

$$\hookrightarrow \text{Product of Sum (POS)} \quad F_2 = (A+B)(\bar{C}+\bar{D})$$

\hookrightarrow Product of Sum (POS) $F_2 = (A+B)(C+D)$
 \hookrightarrow Sum of Product (SOP) $F_1 = (AB) + (\bar{C}D)$

\rightarrow Convert into standard form: (SOP) [Reduce the no. of terms/variables]

$$F_1 = \underbrace{ABC}_{\downarrow} + \underbrace{AB\bar{C}}_{\downarrow} + \underbrace{\bar{A}BC}_{\downarrow} + \underbrace{\bar{A}\bar{B}C}_{\downarrow}$$


$$= AB(\bar{C}+C) + \bar{A}B(C+\bar{C})$$

$$= AB + \bar{A}B$$

$$= B(A+\bar{A})$$

$$= \boxed{B}$$

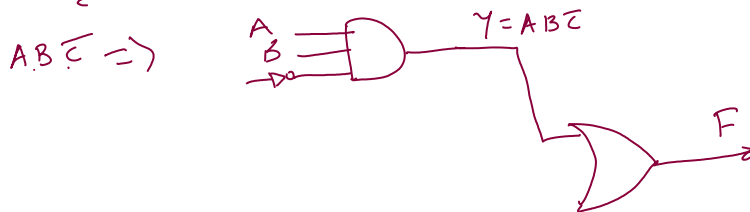Hardware will be more & hence cost of the system will be more.



Exercise:-

(1) Reduce the following functions to minimum no. of literals:

(a) $AB + \bar{A}(B+C) + \bar{B}(B+D) =$

(b) $(X+Y+Z)(\bar{X}+\bar{Y}+\bar{Z})X =$

$= X(\bar{Y}'Z + Z')$
 $= X(\bar{Y} + Z')$

(c) $AB + \bar{A}C + \bar{A}\bar{B}C (AB+C) = 1$

[a]

$AB + \bar{A}(B+C) + \bar{B}(B+D)$

$= AB + \bar{A}B + \bar{A}C + \bar{B}B + \bar{B}D$

$= AB + AC + 0 + \bar{B}D$

$= A(B+C) + \bar{B}D \Rightarrow$

[c] $AB + \bar{A}C + \bar{A}\bar{B}C (AB+C)$

AND - 3
 OR - 3
 NOT - 1

 7

OR - 2
 NOT - 1
 AND - 2

 5

$$= AB + \overline{A} + \overline{C} + (\overline{A}\overline{B}C \cdot AB + A\overline{B}\overline{C} \cdot C)$$

$$= AB + \overline{A} + \overline{C} + A\overline{B}C$$

$$= A(B + \overline{B}C) + \overline{A} + \overline{C}$$

$$= A(B + \overline{B})(B + C) + \overline{A} + \overline{C}$$

$$= AB + \overbrace{AC}^{(AC + \overline{A}C)} + \overline{AC} \Rightarrow (x + \overline{x})$$

$$= AB + 1$$

$$= 1$$

Ex. 4

Prove that:

$$\overline{(A\overline{B} + AB C)} + A(B + A\overline{B}) = 0$$