

EXPERIMENT NO:-6

- **AIM:** To Design and test decoder circuit.
- **APPARATUS:** Trainer kit, connecting wires
- **THEORY:**

Discrete quantities of information are represented in digital systems with binary codes. A binary code of n bits is capable of representing up to 2^n distinct elements of the coded information. A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines. If the n -bit decoded information has unused or don't-care combinations, the decoder output will have less than 2^n outputs.

The decoders presented here are called n -to- m line decoders where $m \leq 2^n$. Their purpose is to generate the 2^n (or less) minterms of n input variables. The name decoder is also used in conjunction with some code such as BCD-to seven -segment decoder.

Consider the 3 to 8 line decoder circuit. The three inputs are decoded into eight outputs. Each output representing one of the minterms of the 3-input variables. The three inverters provide the complement of the outputs, and each one of eight AND gates generate one of the minterms. A particular application of this decoder would be a binary to octal conversion. The input variables may represent a binary number, and the outputs will then represent the eight digits in the octal number system. However a 3-to-8-line decoder can be used for decoding and 3-bit code to provide eight outputs, one for each element of the code.

CIRCUIT DIAGRAM OF 3 TO 8 BIT DECODER:

TRUTH TABLE OF 3 TO 8 BIT DECODER:

INPUTS				OUTPUTS							
ENABLE	ADDRESS LINES										
EN	A2	A1	A0	Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0

➤ **PROCEDURE:**

- (1) First of all apply any combination of 3-bit input.
- (2) Keep the EN1 to high and EN2 to low according to the data sheet.
- (3) Now give all the output Q0 to Q7 to the output indicator LED and verify the truth table.

➤ **CONCLUSION:**

➤ **Exercise:**

Design 4 to 16 decoder using two 3 to 8 decoder.